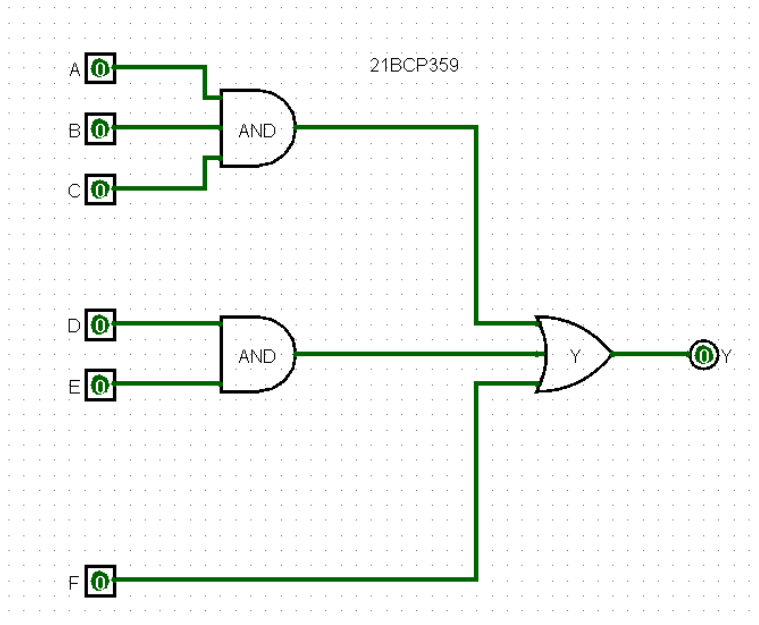


Lab 1: Basic Gate Operations

Question 1: Design the following logic functions using basic gates and test the output using truth table


a. $Y = ABC + DE + F$



A	B	C	D	E	F	Y
0	0	0	0	0	0	0
0	0	0	0	0	1	1
0	0	0	0	1	0	0
0	0	0	0	1	1	1
0	0	0	1	0	0	0
0	0	0	1	0	1	1
0	0	0	1	1	0	1
0	0	0	1	1	1	1
0	0	1	0	0	0	0
0	0	1	0	0	1	1
0	0	1	0	1	0	0
0	0	1	0	1	1	1
0	0	1	1	0	0	0
0	0	1	1	0	1	1
0	0	1	1	1	0	1
0	0	1	1	1	1	1
0	1	0	0	0	0	0
0	1	0	0	0	1	1
0	1	0	0	1	0	0
0	1	0	0	1	1	1
0	1	0	1	0	0	0
0	1	0	1	0	1	1
0	1	0	1	1	0	1
0	1	0	1	1	1	1
0	1	1	0	0	0	0
0	1	1	0	0	1	1
0	1	1	0	1	0	0
0	1	1	0	1	1	1
0	1	1	1	0	0	0
0	1	1	1	0	1	1
0	1	1	1	1	0	1
0	1	1	1	1	1	1
1	0	0	0	0	0	0
1	0	0	0	0	1	1
1	0	0	0	1	0	0


1	0	0	0	1	1	1
1	0	0	1	0	0	0
1	0	0	1	0	1	1
1	0	0	1	1	0	1
1	0	0	1	1	1	1
1	0	1	0	0	0	0
1	0	1	0	0	1	1
1	0	1	0	1	0	0
1	0	1	0	1	1	1
1	0	1	1	0	1	1
1	0	1	1	1	0	1
1	0	1	1	1	1	1
1	1	0	0	0	0	0
1	1	0	0	0	1	1
1	1	0	0	1	0	0
1	1	0	0	1	1	1
1	1	0	1	0	0	0
1	1	0	1	0	1	1
1	1	0	1	1	0	1
1	1	0	1	1	1	1
1	1	1	0	0	0	1
1	1	1	0	0	1	1
1	1	1	0	1	0	1
1	1	1	0	1	1	1
1	1	1	1	0	0	1
1	1	1	1	0	1	1
1	1	1	1	1	0	1
1	1	1	1	1	1	1

b. $Z = A'B' + AB' + A'B + AB$

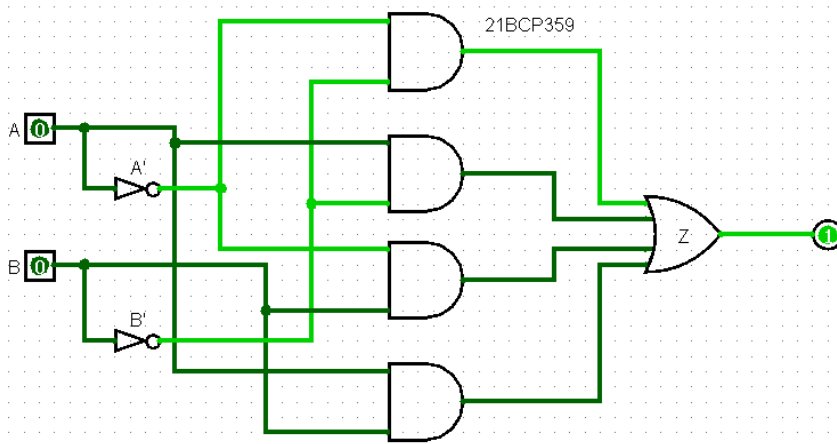

A	B	x
0	0	1
0	1	1
1	0	1
1	1	1


c. $K = (A'+B') (A+B') (A'+B) (A+B)$

 

A	B	K
0	0	0
0	1	0
1	0	0
1	1	0


Question 2: Design the verify the functionality using existing library of basic gates in Logisim.

a. $Y = ((A+B).(C+D+E))'$

 


A	B	C	D	E	Y
0	0	0	0	0	1
0	0	0	0	1	1
0	0	0	1	0	1
0	0	0	1	1	1
0	0	1	0	0	1
0	0	1	0	1	1
0	0	1	1	0	1
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	0	1	0
0	1	0	1	0	0
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	0	1	0
0	1	1	1	0	0
0	1	1	1	1	0
1	0	0	0	0	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	0	1	1	0
1	0	1	0	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	0	0	1	0
1	1	0	1	0	0
1	1	0	1	1	0
1	1	1	0	0	0
1	1	1	0	1	0
1	1	1	1	0	0
1	1	1	1	1	0

b. $F = ((A.B)') + ((A)'(B)')'$

 

A	B	F
0	0	0
0	1	0
1	0	0
1	1	0

 
c. $K = (((A)' + B)') \cdot ((A)' + (B)')'$



A	a	K
0	0	1
0	1	1
1	0	1
1	1	1


Question 3: For each of the following problem statement, design a circuit, describe a Truth table and verify the outcome using Logisim

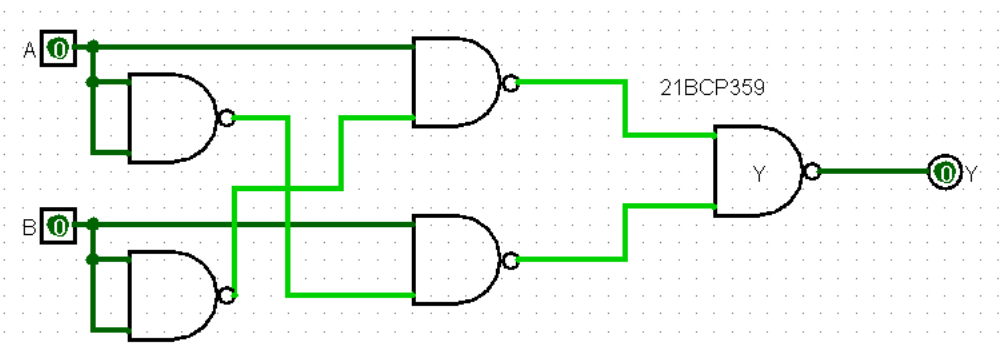a. Implement the functionality of XOR gate using only NAND gates.




A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

 b. Implement the functionality of XNOR gate using only NOR gates.




A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

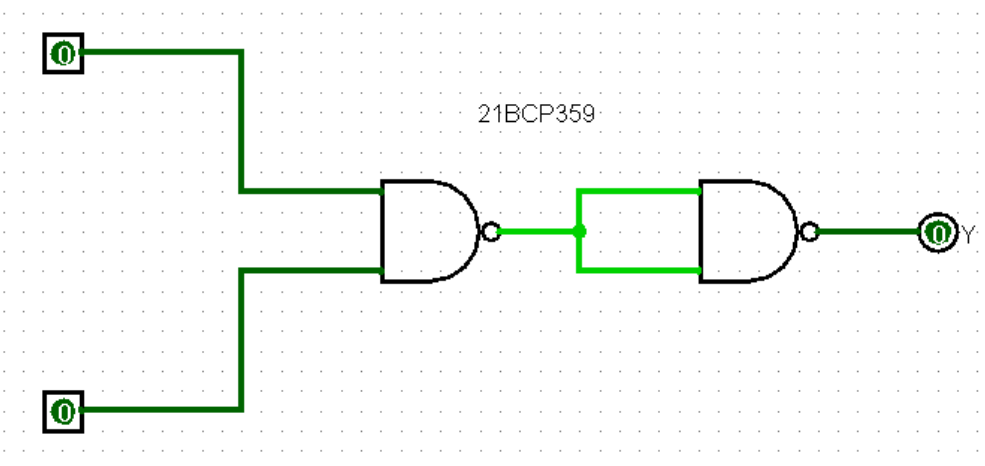c. Implement the functionality of AND gate using only NAND gates.




a	b	Y
0	0	0
0	1	0
1	0	0
1	1	1

 d. Implement the functionality of OR gate using only NOR gates.



a	b	Y
0	0	0
0	1	1
1	0	1
1	1	1

 e. Implement the functionality of NOT gate using only NAND gate.



a	Y
0	1
1	0