

Tutorial – 9 (Questions)

1. Design and Implement a 4-bit binary-to-gray code converter.
2. Design and Implement a 4-bit gray-to-binary code converter.
3. A safe has 5 locks v, w, x, y and z; all of which must be unlocked for the safe to open. The keys to the locks are distributed among 5 executives in the following manner.
 - Mr. A has keys for locks v and x.
 - Mr. B has keys for locks v and y.
 - Mr. C has keys for locks w and y.
 - Mr. D has keys for locks x and z.
 - Mr. E has keys for locks v and z.
 - Mr. A has keys for locks v and x.
 - a. Determine the minimal number of executives required to open the safe.
 - b. Find all the combinations of executives that can open the safe; write an expression $f(A, B, C, D, E)$ which specifies when the safe can be opened as a function of what executives are present?
 - c. Who is essential executive?
4. The input to computer circuit are the 4-bits of the binary number $A_3A_2A_1A_0$. The circuit is required to produce a 1 if and only if all of the following conditions hold.
 - a. The MSB is a 1 or any of the other bits are a 0.
 - b. A_2 is a 1 or any of the other bits are a 0.
 - c. Any of the 4 bits are a 0.Obtain a minimal expression.
5. You are presented with a set of requirements under which an insurance policy can be issued. The applicant must be:
 - a. A married female 25 years old or over, or
 - b. A female under 25, or
 - c. A married male under 25 who has not been involved in a car accident, or
 - d. A married male who has been involved in a car accident, or
 - e. A married male 25 years or above who has not been involved in a car accident.Find the algebraic expression which assumes a value 1 whenever the policy is issued. Simplify the expression obtained.