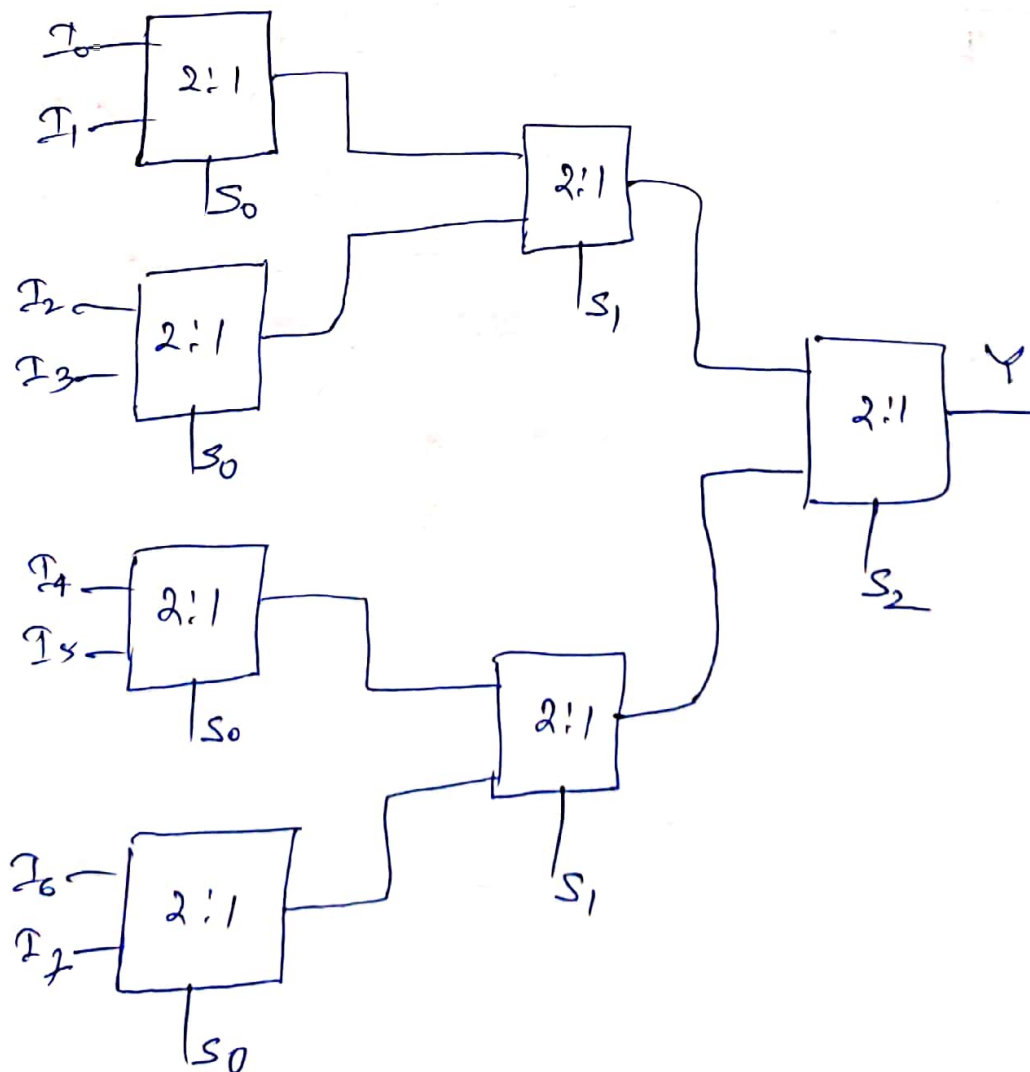



①

Tutorial - 10 (Solutions)

S_2	S_1	S_0	Y
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7




 ② Using enable input we have to implement it.



③

A	S_2 B	S_1 C	S_0 D	F	Value of F	For both occurrences of
0	0	0	0	1	\overline{A}	BCD = 000
0	0	0	1	1	\overline{A}	BCD = 001
0	0	1	0	1	1	BCD = 010
0	0	1	1	1	1	BCD = 011
0	1	0	0	1	\overline{A}	BCD = 100
0	1	0	1	0	0	BCD = 101
0	1	1	0	0	A	BCD = 110
0	1	1	1	0	A	BCD = 111
1	0	0	0	0	\overline{A}	BCD = 000
1	0	0	1	0	\overline{A}	BCD = 001
1	0	1	0	1	1	BCD = 010
1	0	1	1	1	1	BCD = 011
1	1	0	0	0	\overline{A}	BCD = 100
1	1	0	1	0	0	BCD = 101
1	1	1	0	1	A	BCD = 110
1	1	1	1	1	A	BCD = 111

 


The truth table for the given function, is shown above. Since the given function is of 4 variables, we can use a multiplexer with three data inputs. This is shown in the figure above.

As seen from the table, since F is different for each of the two occurrences of $BCD = 000$, $BCD = 001$, and $BCD = 100$, and since $F = \bar{A}$ in each such case, A is connected to the data inputs of D_0 , D_1 , and D_4 .

Since F is different for each of the two occurrences of $BCD = 110$ and $BCD = 111$, and since $F = A$ in both cases, A is connected to D_6 and D_7 . Since F is the same for each of the two occurrences of $BCD = 010$ and $BCD = 011$, and $F = 1$ in both cases, 1 is connected to D_2 and D_3 . and

Since F is same for both the occurrences of $BCD = 101$, and since $F = 0$ in both the cases, 0 is connected to D_5 . The corresponding logic diagram is given above.

④

 


The truth table for F and the logic diagram to implement F are shown above. Since there are three input variables, we can use a multiplexer with three data select inputs (8 to 1 MUX). The truth table shows the use of data select inputs S_2 , S_1 , and S_0 for input variables A, B and C respectively.

Since $F=1$ when $ABC = 001, 010, 100$ and 111 , we connect logical 1 to data inputs D_1, D_2, D_4 , and D_7 .

Logical 0 is connected to other data inputs D_0, D_3, D_5 , and D_6 .

5

 

The realization is shown in Figure above. The decoder's outputs are active LOW; therefore, a NAND gate is required for every output of the combinational circuit.