 


Tutorial – 12 (Questions)

1. Construct a JK flip-flop using a D flip-flop, a two-to-one-line multiplexer, and an inverter.
2. A PN flip-flop has four operations: clear to 0, no change, complement, and set to 1, when inputs P and N are 00, 01, 10, and 11, respectively.
 - a. Tabulate the characteristic table.
 - b. Tabulate the excitation table.
 - c. Derive the characteristic equation.
 - d. Show how the PN flip-flop can be converted to a D flip-flop.
3. Show that the characteristic equation for the complement output of a JK flip-flop is
$$Q'(t + 1) = J'Q' + KQ$$
4. Draw the wave form for Q and Q' for the SR flip flop assuming clock is high.



5. Implement SR latch using NAND gates and realize it for the following cases. Finally, write the truth table.
 - a. S=0 and R=0
 - b. S=0 and R=1
 - c. S=1 and R=0
 - d. S=1 and R=1