

Tutorial-7

①

Q1 Consider a 3-variable function $f(x, y, z) = \sum (3, 5, 6)$. It is minimized as $x + yz$. What are the don't cares used in this minimization.

Q2 Consider the following K-MAP.


| $wx \backslash yz$ | 00 | 01 | 11 | 10 |
|--------------------|----|----|----|----|
| 00 | 1 | | | 1 |
| 01 | 1 | 1 | 1 | 1 |
| 11 | 1 | | | 1 |
| 10 | 1 | 1 | 1 | 1 |

Find all the minimal expression denoted by the above K-MAP.


Q3 Let α, β, γ denotes don't cares. What will be their values in the minimization of sum of product expression.

| $wx \backslash yz$ | 00 | 01 | 11 | 10 |
|--------------------|---------|----------|----------|----|
| 00 | 0 | 0 | α | 0 |
| 01 | 0 | 0 | 1 | 1 |
| 11 | 1 | 1 | 1 | 1 |
| 10 | β | γ | 0 | 0 |

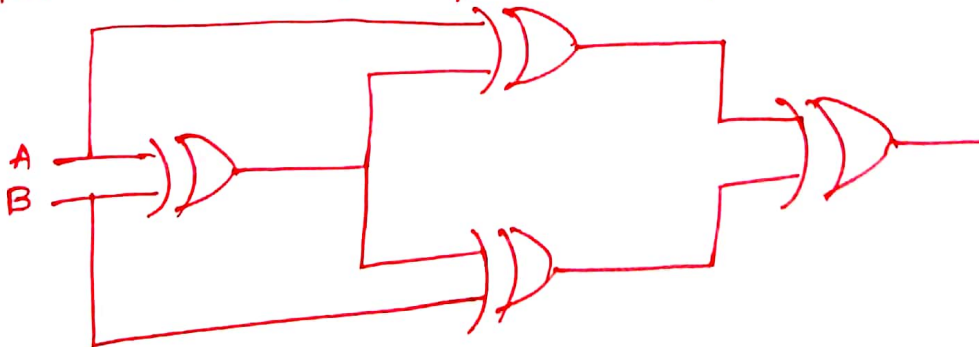Q4 What is the expression represented by following combination.



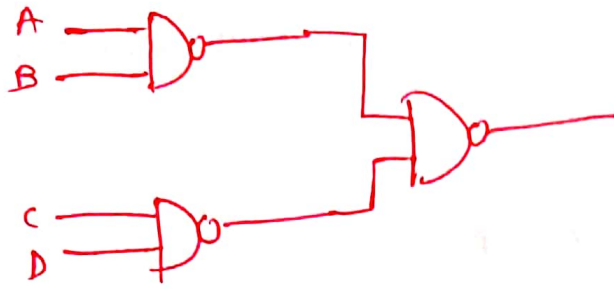Q5/ What is the function represented by the following realization. (2)



Q6/ What is the value of α and β if the following expression is solved.

$$\begin{array}{r} (\alpha 5 6 7)_8 \\ + (2 \beta \alpha 5)_8 \\ \hline (7 1 \beta \alpha)_8 \end{array}$$

Q7/ Implement half adder using universal logic (i.e. NAND and NOR).